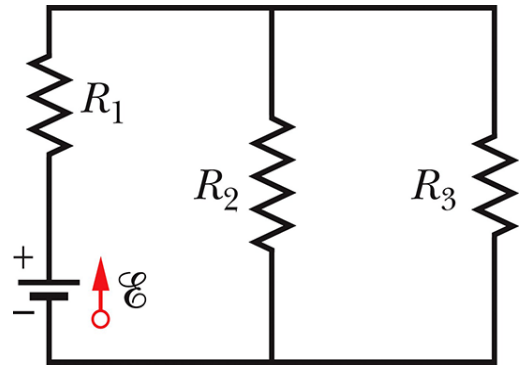


Phyx 135-2, Fall 2016, Quiz #3
Lecture Section 02 (1 pm)

Name _____

1) (12 points) In the circuit at right, the ideal battery has an emf of 12 volts. $R_1 = 15 \Omega$, $R_2 = 20 \Omega$, and $R_3 = 10 \Omega$. What is the current flowing through R_2 ?

Solution: First we must calculate the current in the circuit. R_2 and R_3 are in parallel, so their equivalent resistance is $1/R = 1/20 + 1/10$, or $R = 20/3 = 6.67 \Omega$. Adding this to R_1 gives a total series resistance of 21.67Ω , which means the current is $12 = i(21.67)$, or $i = 0.554$ amps.




The voltage drop across R_1 is thus $(0.554)(15) = 8.3$ volts, so the voltage drop across R_2 and R_3 must be $12 - 8.3 = 3.7$ volts. We have $3.7 = i(20)$, or $i = 0.185$ amps.

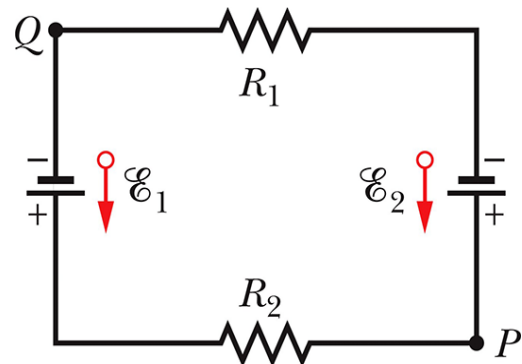2) (8 points) In the circuit at right, suppose $\mathcal{E}_1 = 9$ v, $\mathcal{E}_2 = 12$ v, $R_1 = 10 \Omega$, and R_2 is an unknown resistance. If the power being dissipated by $R_1 = 0.5$ watts, then what is the resistance of R_2 ?

Solution

The current flowing in R_1 must satisfy the relation $P = i^2R$, so we have $0.5 = i^2(10)$, or $i = 0.224$ amp.



For the entire circuit, we require that $12 - 9 = (0.224)(10 + R_2)$, so $R_2 = 3.4 \Omega$.