

23. Let  $i_1$  be the current in  $R_1$  and take it to be positive if it is to the right. Let  $i_2$  be the current in  $R_2$  and take it to be positive if it is upward.

(a) When the loop rule is applied to the lower loop, the result is

$$\varepsilon_2 - i_1 R_1 = 0 .$$

The equation yields

$$i_1 = \frac{\varepsilon_2}{R_1} = \frac{5.0 \text{ V}}{100 \Omega} = 0.050 \text{ A} .$$

(b) When it is applied to the upper loop, the result is

$$\varepsilon_1 - \varepsilon_2 - \varepsilon_3 - i_2 R_2 = 0 .$$

The equation gives

$$i_2 = \frac{\varepsilon_1 - \varepsilon_2 - \varepsilon_3}{R_2} = \frac{6.0 \text{ V} - 5.0 \text{ V} - 4.0 \text{ V}}{50 \Omega} = -0.060 \text{ A} ,$$

or  $|i_2| = 0.060 \text{ A}$ . The negative sign indicates that the current in  $R_2$  is actually downward.

(c) If  $V_b$  is the potential at point  $b$ , then the potential at point  $a$  is  $V_a = V_b + \varepsilon_3 + \varepsilon_2$ , so

$$V_a - V_b = \varepsilon_3 + \varepsilon_2 = 4.0 \text{ V} + 5.0 \text{ V} = 9.0 \text{ V} .$$

27. Since the potential differences across the two paths are the same,  $V_1 = V_2$  ( $V_1$  for the left path, and  $V_2$  for the right path), we have  $i_1 R_1 = i_2 R_2$ , where  $i = i_1 + i_2 = 5000 \text{ A}$ . With  $R = \rho L / A$  (see Eq. 26-16), the above equation can be rewritten as

$$i_1 d = i_2 h \quad \Rightarrow \quad i_2 = i_1 (d / h) .$$

With  $d / h = 0.400$ , we get  $i_1 = 3571 \text{ A}$  and  $i_2 = 1429 \text{ A}$ . Thus, the current through the person is  $i_1 = 3571 \text{ A}$ , or approximately 3.6 kA.

29. (a) The parallel set of three identical  $R_2 = 18 \Omega$  resistors reduce to  $R = 6.0 \Omega$ , which is now in series with the  $R_1 = 6.0 \Omega$  resistor at the top right, so that the total resistive load across the battery is  $R' = R_1 + R = 12 \Omega$ . Thus, the current through  $R'$  is  $(12\text{V})/R' = 1.0 \text{ A}$ , which is the current through  $R$ . By symmetry, we see one-third of that passes through any one of those  $18 \Omega$  resistors; therefore,  $i_1 = 0.333 \text{ A}$ .

(b) The direction of  $i_1$  is clearly rightward.

(c) We use Eq. 26-27:  $P = i^2 R' = (1.0 \text{ A})^2(12 \ \Omega) = 12 \text{ W}$ . Thus, in 60 s, the energy dissipated is  $(12 \text{ J/s})(60 \text{ s}) = 720 \text{ J}$ .

30. Using the junction rule ( $i_3 = i_1 + i_2$ ) we write two loop rule equations:

$$10.0 \text{ V} - i_1 R_1 - (i_1 + i_2) R_3 = 0$$

$$5.00 \text{ V} - i_2 R_2 - (i_1 + i_2) R_3 = 0.$$

(a) Solving, we find  $i_2 = 0$ , and

(b)  $i_3 = i_1 + i_2 = 1.25 \text{ A}$  (downward, as was assumed in writing the equations as we did).

33. First, we note in  $V_4$ , that the voltage across  $R_4$  is equal to the sum of the voltages across  $R_5$  and  $R_6$ :

$$V_4 = i_6(R_5 + R_6) = (1.40 \text{ A})(8.00 \ \Omega + 4.00 \ \Omega) = 16.8 \text{ V}.$$

The current through  $R_4$  is then equal to  $i_4 = V_4/R_4 = 16.8 \text{ V}/(16.0 \ \Omega) = 1.05 \text{ A}$ .

By the junction rule, the current in  $R_2$  is

$$i_2 = i_4 + i_6 = 1.05 \text{ A} + 1.40 \text{ A} = 2.45 \text{ A},$$

so its voltage is  $V_2 = (2.00 \ \Omega)(2.45 \text{ A}) = 4.90 \text{ V}$ .

The loop rule tells us the voltage across  $R_3$  is  $V_3 = V_2 + V_4 = 21.7 \text{ V}$  (implying that the current through it is  $i_3 = V_3/(2.00 \ \Omega) = 10.85 \text{ A}$ ).

The junction rule now gives the current in  $R_1$  as  $i_1 = i_2 + i_3 = 2.45 \text{ A} + 10.85 \text{ A} = 13.3 \text{ A}$ , implying that the voltage across it is  $V_1 = (13.3 \text{ A})(2.00 \ \Omega) = 26.6 \text{ V}$ . Therefore, by the loop rule,

$$\mathcal{E} = V_1 + V_3 = 26.6 \text{ V} + 21.7 \text{ V} = 48.3 \text{ V}.$$

36. (a) Using the junction rule ( $i_1 = i_2 + i_3$ ) we write two loop rule equations:

$$\mathcal{E}_1 - i_2 R_2 - (i_2 + i_3) R_1 = 0$$

$$\mathcal{E}_2 - i_3 R_3 - (i_2 + i_3) R_1 = 0.$$

Solving, we find  $i_2 = 0.0109 \text{ A}$  (rightward, as was assumed in writing the equations as we did),  $i_3 = 0.0273 \text{ A}$  (leftward), and  $i_1 = i_2 + i_3 = 0.0382 \text{ A}$  (downward).

(b) The direction is downward. See the results in part (a).

(c)  $i_2 = 0.0109 \text{ A}$  . See the results in part (a).

(d) The direction is rightward. See the results in part (a).

(e)  $i_3 = 0.0273 \text{ A}$ . See the results in part (a).

(f) The direction is leftward. See the results in part (a).

(g) The voltage across  $R_1$  equals  $V_A$ :  $(0.0382 \text{ A})(100 \Omega) = +3.82 \text{ V}$ .