

35. The resistance of the coil is related to the reactances and the phase constant by Eq. 31-65. Thus,

$$\frac{X_L - X_C}{R} = \frac{\omega_d L - 1/\omega_d C}{R} = \tan \phi ,$$

which we solve for  $R$ :

$$R = \frac{1}{\tan \phi} \left( \omega_d L - \frac{1}{\omega_d C} \right) = \frac{1}{\tan 75^\circ} \left[ (2\pi)(930 \text{ Hz})(8.8 \times 10^{-2} \text{ H}) - \frac{1}{(2\pi)(930 \text{ Hz})(0.94 \times 10^{-6} \text{ F})} \right] \\ = 89 \Omega .$$

36. (a) The circuit has a resistor and a capacitor (but no inductor). Since the capacitive reactance decreases with frequency, then the asymptotic value of  $Z$  must be the resistance:  $R = 500 \Omega$ .

(b) We describe three methods here (each using information from different points on the graph):

method 1: At  $\omega_d = 50 \text{ rad/s}$ , we have  $Z \approx 700 \Omega$ , which gives  $C = (\omega_d \sqrt{Z^2 - R^2})^{-1} = 41 \mu\text{F}$ .

method 2: At  $\omega_d = 50 \text{ rad/s}$ , we have  $X_C \approx 500 \Omega$ , which gives  $C = (\omega_d X_C)^{-1} = 40 \mu\text{F}$ .

method 3: At  $\omega_d = 250 \text{ rad/s}$ , we have  $X_C \approx 100 \Omega$ , which gives  $C = (\omega_d X_C)^{-1} = 40 \mu\text{F}$ .

37. The rms current in the motor is

$$I_{\text{rms}} = \frac{\mathcal{E}_{\text{rms}}}{Z} = \frac{\mathcal{E}_{\text{rms}}}{\sqrt{R^2 + X_L^2}} = \frac{420 \text{ V}}{\sqrt{(45.0 \Omega)^2 + (32.0 \Omega)^2}} = 7.61 \text{ A} .$$

53. (a) Using Eq. 31-61, the impedance is

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{(12.0 \Omega)^2 + (1.30 \Omega - 0)^2} = 12.1 \Omega .$$

(b) The average rate at which energy has been supplied is

$$P_{\text{avg}} = \frac{\mathcal{E}_{\text{rms}}^2 R}{Z^2} = \frac{(120 \text{ V})^2 (12.0 \Omega)}{(12.07 \Omega)^2} = 1.186 \times 10^3 \text{ W} \approx 1.19 \times 10^3 \text{ W} .$$

56. (a) The power consumed by the light bulb is  $P = I^2 R/2$ . So we must let  $P_{\text{max}}/P_{\text{min}} = (I/I_{\text{min}})^2 = 5$ , or

$$\left(\frac{I}{I_{\min}}\right)^2 = \left(\frac{\mathcal{E}_m / Z_{\min}}{\mathcal{E}_m / Z_{\max}}\right)^2 = \left(\frac{Z_{\max}}{Z_{\min}}\right)^2 = \left(\frac{\sqrt{R^2 + (\omega L_{\max})^2}}{R}\right)^2 = 5.$$

We solve for  $L_{\max}$ :

$$L_{\max} = \frac{2R}{\omega} = \frac{2(120\text{ V})^2 / 1000\text{ W}}{2\pi(60.0\text{ Hz})} = 7.64 \times 10^{-2}\text{ H}.$$

(b) Yes, one could use a variable resistor.

(c) Now we must let

$$\left(\frac{R_{\max} + R_{\text{bulb}}}{R_{\text{bulb}}}\right)^2 = 5,$$

or

$$R_{\max} = (\sqrt{5} - 1)R_{\text{bulb}} = (\sqrt{5} - 1)\frac{(120\text{ V})^2}{1000\text{ W}} = 17.8\ \Omega.$$

(d) This is not done because the resistors would consume, rather than temporarily store, electromagnetic energy.

64. For step-up transformer:

(a) The smallest value of the ratio  $V_s / V_p$  is achieved by using  $T_2T_3$  as primary and  $T_1T_3$  as secondary coil:  $V_{13}/V_{23} = (800 + 200)/800 = 1.25$ .

(b) The second smallest value of the ratio  $V_s / V_p$  is achieved by using  $T_1T_2$  as primary and  $T_2T_3$  as secondary coil:  $V_{23}/V_{13} = 800/200 = 4.00$ .

(c) The largest value of the ratio  $V_s / V_p$  is achieved by using  $T_1T_2$  as primary and  $T_1T_3$  as secondary coil:  $V_{13}/V_{12} = (800 + 200)/200 = 5.00$ .

For the step-down transformer, we simply exchange the primary and secondary coils in each of the three cases above.

(d) The smallest value of the ratio  $V_s / V_p$  is  $1/5.00 = 0.200$ .

(e) The second smallest value of the ratio  $V_s / V_p$  is  $1/4.00 = 0.250$ .

(f) The largest value of the ratio  $V_s / V_p$  is  $1/1.25 = 0.800$ .