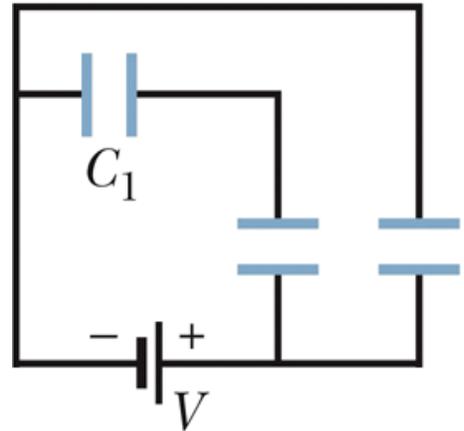


1) In the network at right, $C_1 = 6 \mu\text{F}$ and the other two capacitors have $C = 3 \mu\text{F}$. We have $V = 9$ volts.

1a) (5 points) What is the electrostatic energy contained in C_1 ?

1b) (5 points) Suppose I fill C_1 with a dielectric that has $\kappa = 3.00$ and fill the other two capacitors with a $\kappa = 2.00$ dielectric. (You may assume that they are all parallel plate capacitors.) What would be the electrostatic energy contained in C_1 then?



Solutions

1a) There are several ways to solve this problem. For example, the equivalent capacitance of C_1 plus the capacitor wired to it in series is given by: $1/C_{\text{eq}} = 1/(6 \times 10^{-6}) + 1/(3 \times 10^{-6})$, or $C_{\text{eq}} = 2 \mu\text{F}$. This means that the charge on the equivalent capacitor (and therefore, also the charge on C_1) is $q = CV = (2 \mu\text{F})(9 \text{ v}) = 18 \mu\text{C}$. We then have $U = \frac{1}{2} q^2/C_1 = (0.5)(18 \times 10^{-6})^2 / (6 \times 10^{-6}) = 2.7 \times 10^{-5} \text{ J}$.

Another way to solve the problem is to realize that C_1 has double the capacitance of its series partner, therefore it must have half the voltage across it, or 3 v. (The partner has 6 v.) We then have $U = \frac{1}{2} CV^2 = (0.5)(6 \mu\text{F})(3 \text{ v})^2 = 2.7 \times 10^{-5} \text{ J}$.

1b) The capacitance of C_1 becomes $18 \mu\text{F}$ and the one wired to it in series becomes $C = 6 \mu\text{F}$. Their equivalent capacitance is then: $1/C_{\text{eq}} = 1/(18 \times 10^{-6}) + 1/(6 \times 10^{-6})$, or $C_{\text{eq}} = 4.5 \mu\text{F}$. Similarly to part (a), this gives us a charge on C_1 of $q = (4.5 \mu\text{F})(9 \text{ v}) = 40.5 \mu\text{C}$. We then have $U = \frac{1}{2} (40.5 \times 10^{-6})^2 / (18 \times 10^{-6}) = 4.56 \times 10^{-5} \text{ J}$.

2) (5 points) Suppose we have a copper wire of radius 0.3 mm which is 1000 m long. And, suppose we have an aluminum wire of unknown radius that is also 1000 m long. What radius would the aluminum wire need to be if it is to have the same resistance as the copper wire?

resistivity of copper = $1.69 \times 10^{-8} \Omega \text{ m}$

resistivity of aluminum = $2.75 \times 10^{-8} \Omega \text{ m}$

Solution

The resistance of the wires is given by $\rho L/A$. In this case we want the resistances to be equal, so we have $\rho_{\text{Cu}} L_{\text{Cu}} / A_{\text{Cu}} = \rho_{\text{Al}} L_{\text{Al}} / A_{\text{Al}}$, or $A_{\text{Al}} = (\rho_{\text{Al}} / \rho_{\text{Cu}}) A_{\text{Cu}}$. The cross-sectional areas of the wires are proportional to πr^2 , so we have $r_{\text{Al}} = (\rho_{\text{Al}} / \rho_{\text{Cu}})^{1/2} r_{\text{Cu}} = (2.75 / 1.69)^{1/2} (0.3 \text{ mm}) = 0.383 \text{ mm}$.

3) (5 points) A parallel-plate capacitor is filled with a $\kappa = 5.5$ dielectric. The area of each plate is 0.034 m^2 and the plates are separated by 2.0 mm. The capacitor will fail (short out) if the electric field between the plates exceeds 200 kN/C . What is the maximum energy that the capacitor can store?


Solution

Since $V = Ed$, we see that the maximum voltage the capacitor can sustain is $(2 \times 10^5)(0.002) = 400 \text{ v}$. We have $U = \frac{1}{2} CV^2$ with $C = \kappa \epsilon_0 A/d$, so $U = \frac{1}{2} (5.5)(8.85 \times 10^{-12})(0.034)/(0.002) \times 400^2 = 6.6 \times 10^{-5} \text{ J}$.

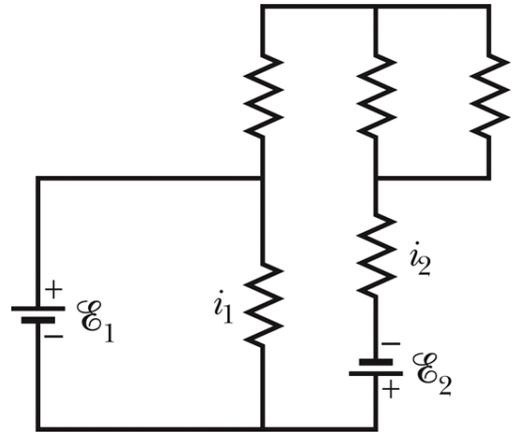4) (10 points) In the network at right, $\mathcal{E}_1 = 6$ v, $\mathcal{E}_2 = 9$ v, and all of the resistors are 5Ω . What are the values of currents i_1 and i_2 , and are they going up or down through their respective resistors?

Solution

The two resistors at top right can be replaced by one equivalent resistor. Its resistance is $1/R = 1/5 + 1/5$, or $R = 2.5 \Omega$. Then this resistance can be placed in series with the resistors on either side of it, to give $R = 12.5 \Omega$. In short, we can reduce the network to just two resistors (labelled by i_1 and i_2), which have resistances of 5 and 12.5Ω , respectively.



We can then write down two loop equations. For the left loop, starting at the battery and going clockwise, we have: $6 - (i_1 - i_2)(5) = 0$. For the right loop, starting at the battery and going clockwise, we have: $9 - (i_2 - i_1)(5) - i_2(12.5) = 0$. There are many ways to do the algebra from here, but probably the simplest is just to add the two equations to get: $15 - 0 - i_2(12.5) = 0$, or $i_2 = 1.2$ amps. The positive sign means i_2 is going down. Going back to the first equation, we have: $6 - (i_1 - 1.2)(5) = 0$, or $i_1 = 2.4$ amps. The positive sign means i_1 is going down.

Therefore the i_1 (as defined on the diagram) is 2.4 amps down minus 1.2 amps up = 1.2 amps down.

5) Suppose you have a cyclotron which has a radius of 53 cm and is capable of maintaining a uniform magnetic field of 1.20 Tesla. The voltage difference between the two halves of the cyclotron is 80 kV. A radioactive source at the exact center of the cyclotron is injecting α -particles into it at approximately zero velocity. (The mass of the α -particle is 6.68×10^{-27} kg. It has a charge of $2e$.)

5a) (5 points) Estimate the maximum energy (in eV) that the α -particles emerging from this cyclotron can achieve.

Solution

By equating mv^2/r (centrifugal force) to the Lorentz force, qvB , we know that $v = qBr/m$ for any radius. The maximum velocity will occur at maximum radius, so $v_{\max} = (2)(1.6 \times 10^{-19})(1.2)(0.53) / (6.68 \times 10^{-27}) = 3.05 \times 10^7$ m/s. This corresponds to $\frac{1}{2} (6.68 \times 10^{-27})(3.05 \times 10^7)^2 / (1.6 \times 10^{-19}) = 19.4$ MeV.

5b) (5 points) About how long does it take for the α -particle to achieve this energy inside the cyclotron?

Solution

We know that $f(2\pi r) = v$, where f is the frequency of revolution, so $f(2\pi r) = qBr/m$, or $f = qB/2\pi m = (3.2 \times 10^{-19})(1.2) / 2\pi (6.68 \times 10^{-27}) = 9.14 \times 10^6$ Hz. This corresponds to the α -particle taking $1 / 9.14 \times 10^6 = 1.09 \times 10^{-7}$ s to make one cycle. Now, the α -particle will gain 2×80 kV of energy each time it makes a cycle, so it needs about $(19.4 \times 10^6) / (160 \times 10^3) = 121$ cycles to gain its full energy. The total time to achieve E_{\max} is then $(1.09 \times 10^{-7} \text{ s})(121) = 1.32 \times 10^{-5}$ s.